

# Build A Microphone Preamp

W. J. J. Hoge

Some of the Gentle Readers of *Audio* who remember my previous articles may be wondering what a loudspeaker engineer is doing writing about microphone preamplifiers. After all, the two devices are at just about the opposite ends of an audio system. Long before I worked with loudspeakers, I worked in the recording industry here in Nashville. Part of my background includes experience as a circuit designer, and I have also worked as a recording engineer. When I decided to move back home to Nashville, I decided to combine those two parts of my background so I am now working with a company which builds large, sophisticated recording consoles.

The quality of recording equipment has been significantly improved over the past few years. When I first started mixing records (back in the '60s), the equipment did not perform especially well by today's standards. For example, it was not uncommon for equipment with rated distortion of 0.5 per-


cent to be considered not only acceptable but pretty damn good. The state of the art has advanced well beyond that.

Today every record you listen to has at least one thing in common with all others. Whether it's from a modern, multi-track studio recording or one made on location using simple techniques, the signals from the microphones had to be amplified before they could be used to drive the tape recorder or (in the case of the music business' most recent giant step backward) the disc cutter-head amplifier directly. The serious amateur recordist does not have much available to him in the way of microphone preamplifiers which meet the standards of those in modern studio equipment. In this article I'll describe one which you can build. It is suitable for use with all common types of microphones with low impedance outputs.

In amplifying the microphone's signal, the preamplifier must not add any extraneous signals, such as noise or distortion. It also must have sufficient bandwidth to pass all the useful information which comes from the microphone, but it should also have a limited bandwidth to help prevent unwanted signals (such as radio frequency interference) from

Harrison Systems, Inc.,  
Nashville, Tenn. 37202

Fig. 1—Schematic of microphone preamp.

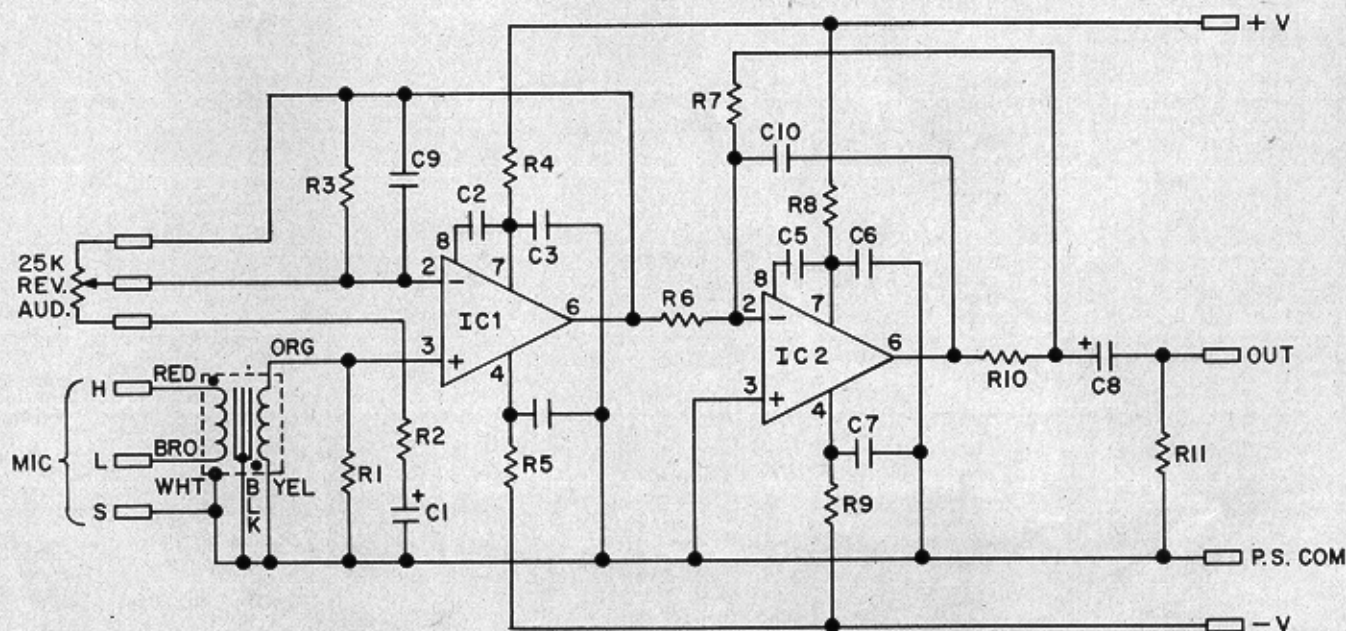

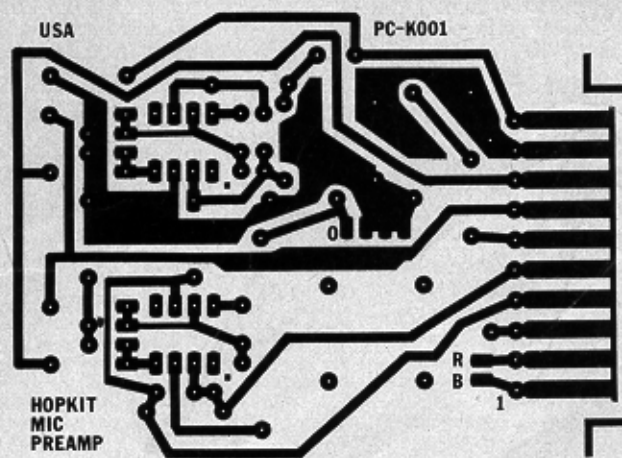


Fig. 2—Pattern, at one-to-one size, for circuit board.

entering the system. For naturally occurring musical signals, the lowest frequency commonly generated is about 41 Hz, however, the lowest tone which comes from a piano is 27.5 Hz. A professional-grade device should be able to pass that piano fundamental. The upper limit of the ear's spectrum is on the order of 20 kHz in young people with good hearing. Information theory tells us that if we try to transmit more information than the receiving end of a system can use, we are wasting our time. Thus, response to 20 kHz is adequate.

Professional-grade microphones of varying types provide output signals of widely varying nominal levels. Ribbon microphones often have sensitivities low enough to yield nominal levels on the order of -60 dB (re: 0.775 V). (Author's Note: 0.775 V is one of those quasi-magical numbers which pops up in audio from time to time. A signal with an rms potential of 0.775 V will cause a 600-ohm resistor to dissipate 1 mW of power.) Condenser microphones are commonly available with output levels on the order of -30 dB. Thus, it is obvious

to the most casual observer that a wide range of gain adjustment should be available in our preamplifier. Usually a gain of +60 dB is good with ribbon microphones; a gain of +20 is about what is required with condenser microphones placed near loud sources. We now have a set of design specifications for our preamplifier. The bandwidth should be from 27.5 Hz to 20 kHz, the gain from +20 to +60 dB, the distortion and noise held to minimum levels, and the input impedance should be compatible with low-impedance microphones. As an additional specification, we ought to specify the output signal level available and the minimum load impedance. Let us say that the preamplifier should be capable of delivering an rms signal of 6 V when operating into a 600-ohm load.


Most high-quality preamplifiers use input transformers. An input transformer which is properly designed can perform several useful functions. First, it can serve as an impedance-matching device between the microphone in the input stage of the amplifier. The purpose of this match is not to achieve maximum power transfer but rather to minimize noise generated in the input stage. There is an optimum range of source impedances for any particular amplifier for best signal-to-noise ratio. Low-impedance microphones have output impedances well below the optimum range for most devices.

A second function that the transformer can perform is limiting the bandwidth of the input signal. Transformers exhibit both low and high frequency roll-off. This can reduce low frequency disturbances from such sources as traffic rumble and high frequency disturbances from such sources as your local Citizens Band (CB).

Finally, a transformer can provide voltage gain. In fact, an input transformer that would properly match the output impedance of a microphone to the impedance of a typical input stage required for best noise performance, would be a step-up transformer.

The particular input transformer selected for this preamplifier is the JE-115K-E made by Jensen Transformers. It has extremely low leakage inductance. When its secondary is loaded with 10 times its characteristic impedance, it exhibits very

Fig. 3—Component placement on circuit board.

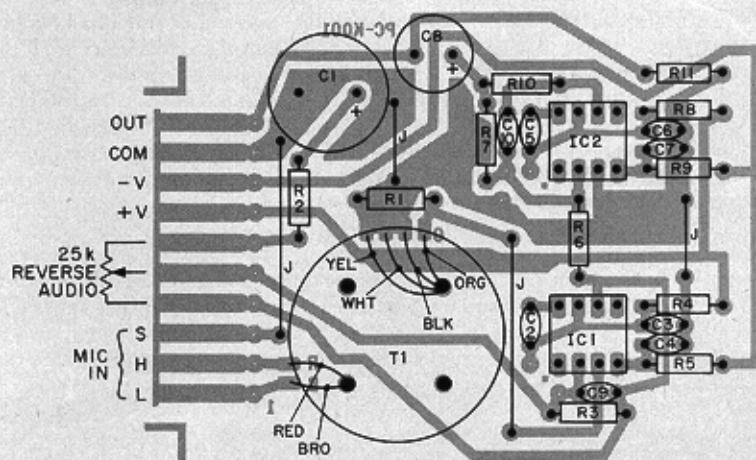



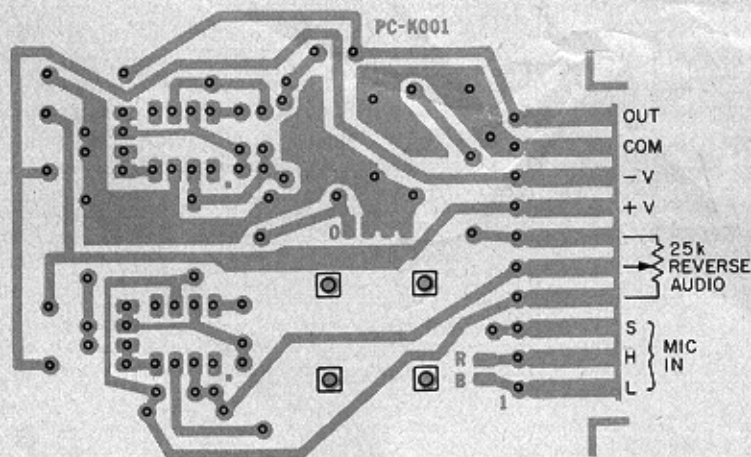


Fig. 4—All holes should be drilled with a #60 bit except the four transformer holes in the squares which should be made with an eighth-inch bit.

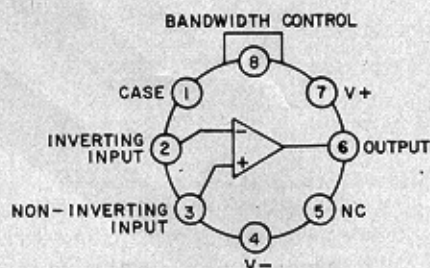


Fig. 5—Pin locations on the 911 op-amp. Caution should be used with these devices as they are sensitive to electrostatic charges.

low overshoot and does not require an RC resonance damping network when it is used with an amplifier with a two- $\mu$ S lead compensation network in its feedback. The input impedance of the primary is about 1400 ohms when the secondary is terminated with 150 kilohms. This provides a proper termination for low-impedance microphones. The secondary presents a source impedance of about 20 kilohms to the input stage of the amplifier. The rate of distortion increase for low-frequency, high-level signals is very low. The voltage gain is +20 dB.

Based on the characteristics of the input transformer, we can specify the rest of our circuit. We need an amplifier with gain adjustable from 0 to +40 dB, an input stage which operates with low noise when used with a 20-kilohm source, a high-frequency roll-off equivalent to that provided by a two- $\mu$ S phase lead network in its feedback loop, and the capability of delivering a 6-V signal to a 600-ohm load. It is, of course, possible to design an amplifier which uses discrete components which will meet our specifications. However, if we can find an integrated circuit which can be used, we can save a great deal of design time and, perhaps, some money.


ICs have a bad name in the audio business. Some operational amplifiers which were designed for d.c. instrumenta-

tion use have been misapplied to audio purposes for which they were unsuited. There do exist a few monolithic op-amps which can be used (with care) in audio systems. One such amplifier is the Harris 911, which exhibits excellent noise characteristics. It is a wide bandwidth device and is capable of delivering a 7-V signal to a 500-ohm load. Figure 1 shows our microphone preamplifier using the 911.

Note that we have used two of the ICs. The first stage provides the voltage gain not provided by the transformer. The second stage provides the high-frequency response shaping for minimum overshoot.

The first stage has its gain normally set by the 25-kilohm reverse audio-taper pot shown in the schematic. When the wiper of the pot is at the bottom, the stage's gain is set by the ratio of the total resistance of the pot to R2. This is 100 to 1 or +40 dB. When the wiper is at the top, the gain is unity. R3 provides feedback around the op-amp at all times. If the pot were not connected or if the wiper were to lift from element of the pot during rotation, the gain of the stage would drop to unity. In the case of the lifting wiper (a not untypical imperfection even in a good pot), the momentary gain drop is less ear shattering than a momentary gain rise to the open-loop gain of the op-amp.

Fig. 6—Shape and hole locations of Jensen transformer.

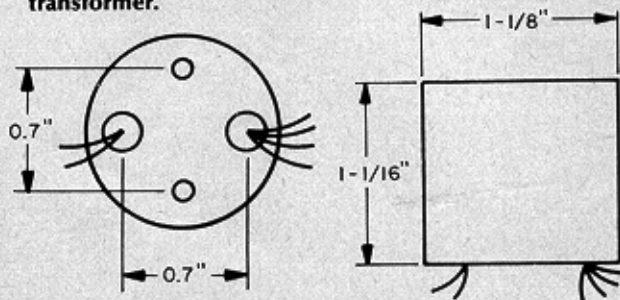

MOUNTING HOLES  
CLEARANCE FOR #4 SCREW  
LEAD HOLES  
USE 0.35" HOLE TO CLEAR GROMMET

Fig. 7—Set up for DIM 100 test. The output of the square-wave generator is bandlimited at 100 kHz.

